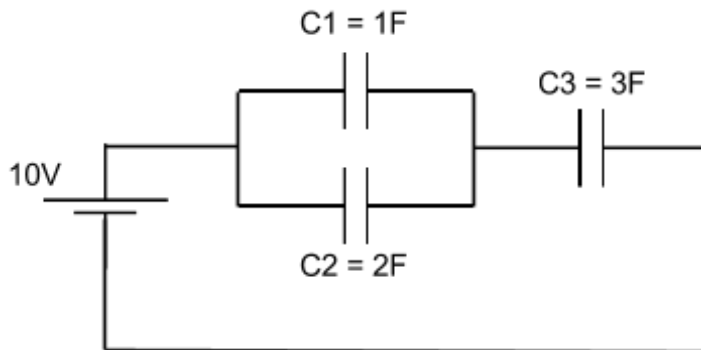


Capacitor Example (for a network of capacitors)

Calculate the total potential energy stored in the capacitors in the circuit.



Solution

Step 1: Replace all capacitors with a single equivalent capacitor.


To calculate the equivalent capacitance, recall that for capacitors in parallel $C_{equivalent} = \sum C_i$ and for

capacitors in series: $C_{equivalent} = \left[\sum \frac{1}{C_i} \right]^{-1}$

In this circuit, C1 and C2 are in parallel, and together they are in series with C3.

$$C_{equivalent} = \left[\frac{1}{C_1 + C_2} + \frac{1}{C_3} \right]^{-1} = \frac{C_3(C_1 + C_2)}{C_1 + C_2 + C_3} = \frac{3(1+2)}{1+2+3} = \frac{3}{2} \text{ (F)}$$

Step 2: Draw the equivalent circuit.

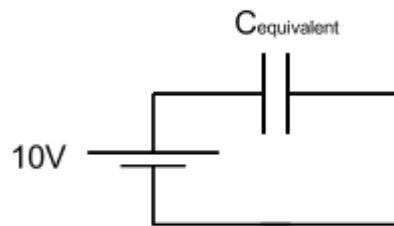

Step 3: Calculate the total potential energy stored in the equivalent capacitor.

Recall that the equation for the energy stored in a capacitor is given by: $U = \frac{CV^2}{2}$

$$\text{Thus, } U_{total} = \frac{C_{equivalent}V^2}{2} = \frac{1.5(10)^2}{2} = 75 \text{ (J)}$$

Answer: The total energy stored in the capacitors is 75 J.