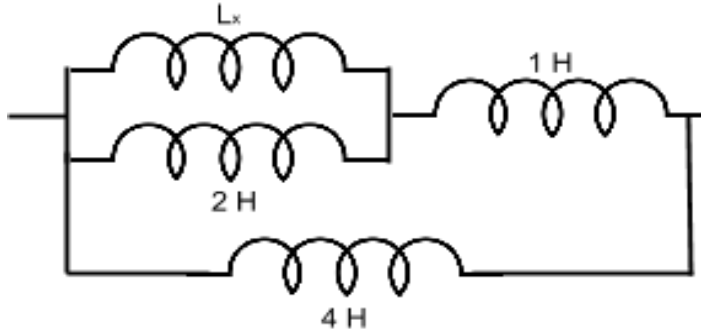


Inductor Example (determine equivalent inductance)

What should the value of the inductance L_x be to yield a total equivalent inductance of $\frac{4}{3} H$?



Solution

Set up an equation for the equivalent inductance, recalling that in series: $L_{equivalent} = \Sigma L_i$ and in

parallel: $L_{equivalent} = \left[\Sigma \left(\frac{1}{L_i} \right) \right]^{-1}$

Let L' be the equivalent inductance of the top 3 inductors: L_x in parallel with the 2_H and together in series with 1_H.

$$L' = \left[\frac{1}{L_x} + \frac{1}{2} \right]^{-1} + 1 \quad \text{Simplifying, we obtain: } L' = \frac{3L_x + 2}{L_x + 2}$$

L' is added in parallel with the 4_H inductor as follows:

$$L_{equivalent} = \left[\frac{1}{4} + \frac{1}{L'} \right]^{-1}$$

Plugging in the expression for L' we obtain: $L_{equivalent} = \frac{4(3L_x + 2)}{7L_x + 10}$

Equating this to the required equivalent inductance of $\frac{4}{3} H$ and solving yields: $L_x = 2 H$

Answer: $L_x = 2 H$